

Besides the voltage and current specifications, the power supplies for AMD Xilinx FPGA power rails must meet the following requirements:

- The output voltage ripple of all power rails (except for analog rails) must be smaller than 10mV in steady state.
- The start-up of all power rails must be monotonic.
- Output voltage deviation of the core rail (VCCINT) must be smaller than $\pm 3\%$ during a 25% load transient at 100A/ μ s.
- The turn-on and turn-off of the power supplies must follow a certain sequence defined by AMD Xilinx.

Rail Name	Voltage (V)	Typ. Max Current (A)	MPS PN (Module)	MPS PN (Discrete)
1	0.72/0.85/0.9	30-50	MPM3695-25 x2	MP8796B x 2
2	0.85/0.9	10-20	MPM3695-25	MP8796B
3	1.8V	5-2	MPM3632C	MP2316
4	1.1-1.5V	1-3	MPM3632C	MP2326
5	1.2	2-4	MPM3695-10	MP2326
6	0.85	0-3	MPM3606A	MP2321
7	1.8	1-0.5	MPM3606A	MP2321
8	0.9	1-2	MPM3632C	MP2316
9	0.925	1.7-2	MPM3833C*/MPM3632C**	MP2316
10	1.8	1-1.3	MPM3833C*/MPM3632C**	MP2316
11	0.925	1-2.2	MPM3683-7	MP2326
12	1.8	0.2-0.5	MPM3833C*/MPM3632C**	MP2316
13	2.5 or 3	0.3-0.6	MPM3833C*/MPM3632C**	MP2316

*Supports up to 6V input voltage, **Supports 12V input voltage. Click for [Complete Discrete Solutions](#).

Table 1: MPS Power Module Solution for AMD Xilinx Zynq UltraScale+RFSoc

Realization of Optimized Power Solution with Power Modules

MPS power modules offer a highly integrated power solution with high efficiency. Figure 2 illustrates the typical structure of MPS’ power modules, which integrate the MPS patented monolithic IC, inductor, and selected passive components in a single molded package. The components are mounted on a lead-frame using Mesh-connect packaging technology, which minimizes thermal resistance between the power IC/inductor and the PCB. The monolithic IC integrates power FETs, a control circuit, and a driver on a single silicon die. Monolithic technology minimizes the parasitic resistance and inductance between the driver circuit and the gate of the power FET. Subsequently, the switching losses are minimized.

Table 1 shows the MPS power module solution for the [AMD Xilinx Zynq UltraScale+ RFSoc](#). Note that a discrete solution is available from MPS.

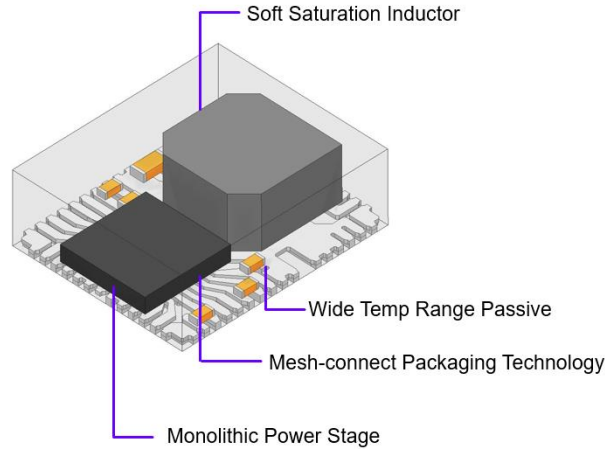


Figure 2: Typical Structure of MPS Power Modules

Figure 3 demonstrates the reference design board for the AMD Xilinx Zynq UltraScale+ RFSoc (exclude the RF data converter rails). The reference design board employs 5 advanced power modules. The [MPM3695-25](#) is a 16V, 20A power module. The core rail utilizes two MPM3695-25s, which are connected in parallel to provide up to 50A peak current. A single MPM3695-25 provides up to 25A peak current for rail 2. The [MPM3695-10](#) is a 14V, 7A ultra-thin power module. The [MPM3632C](#) is an 18V, 3A forced CCM power module.



Figure 3: Reference Design Board for Zynq UltraScale+ RFSoc

Start-up Sequence

Shut-down Sequence

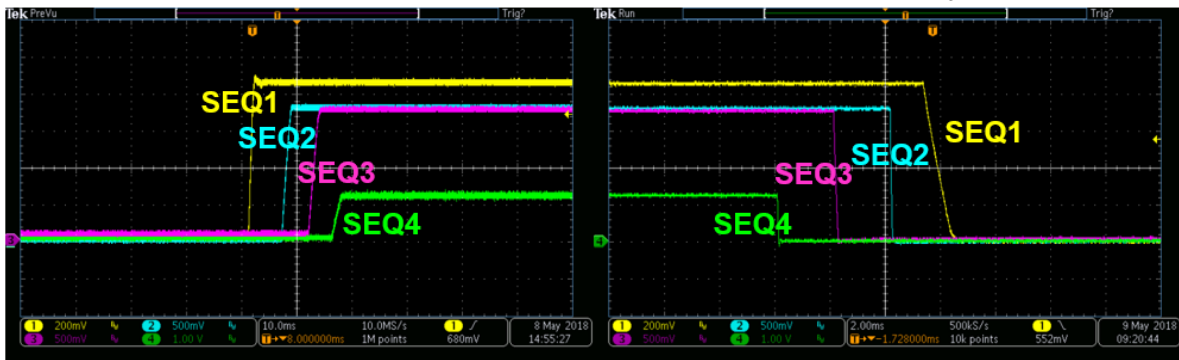



Figure 4: Power-Up and Power-Down Sequence

The [MPM3606A](#) is a 21V, 0.6A power module. The same family also offers pin compatible power modules with 1A, 2A, and 3A power modules, which provide great flexibility in power solution design. The performance of the reference design is fully verified to meet AMD Xilinx requirements. Figure 4 shows the waveform of the power-on and power-off sequence.

The advanced MPM3695 series of power modules with integrated inductors offer a versatile solution for powering FPGAs and ASICs. The output current of the MPM3695 series is scalable by stacking multiple MPM3695-25s or MPM3695-10s. The MPM3695 series offers up to 60% higher power density, compared to discrete point-of-load (POL) solutions, simplified PCB layout and power stage design, minimal external components, and minimal expertise for the power converter and compensation network design. With the monolithic structure of the power IC and customized integrated inductor design with advanced packaging technology, the MPM3695 series power modules reduce the footprint up to 40% compared to competing power modules.

Figure 5 and 6 show the load transient waveform at 25% load transient at 100 μ A/s and the output voltage ripple at full load, respectively. As shown in the figures, the output voltage deviation is below \pm 3% during the load transient, and the output voltage ripple is smaller than 10mV at steady state.

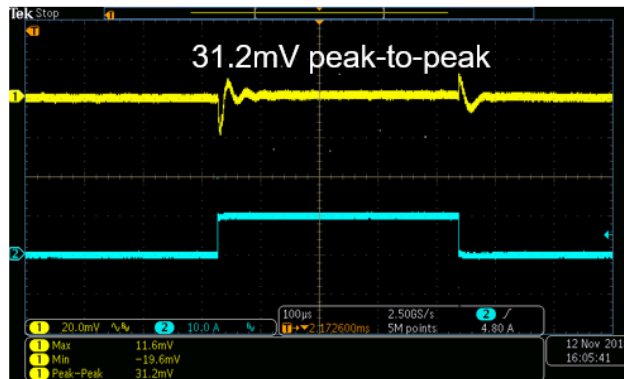
Load Transient Waveform
25% load step at 100A/us



100us/div

Figure 5: Load Transient Waveform of the Core Rail

Output Voltage Ripple at 50A Load

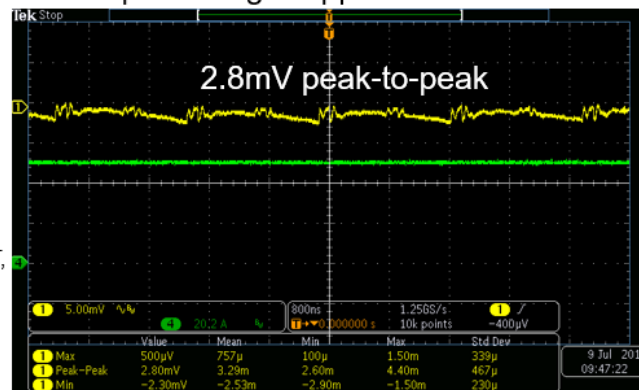


800ns/div

Figure 6: Output Voltage Ripple of the Core Rail

Analog Power Module for ZCU1275

The AMD Xilinx Ultrascale+ RFSoc embeds a high-speed analog to digital converter (ADC) and digital to analog converter (DAC), which require ultra-low output noise. A switch-mode power supply (SMPS) has the advantage of high efficiency compared to traditional low-dropout (LDO) regulators. Due to its switching nature, a SMPS emits noise at its switching frequency and its harmonics.

 The MPS power module solution leverages two-stage CLC filters to minimize the output voltage noise for the sensitive ADC and DAC rails. The EVREF0102A is the RF data converter power module developed for the ZCU1275 Zynq UltraScale+ RFSoc Characterization Kit. Figure 7 demonstrates the EVREF0102 power module.



MPS EVREF0102 Power Module

- Full module solution
- Power RF 12-bit 2GSPS ADCs and 14-bit 6.4GSPS DACs rails
- Ultra-low noise: <1mV Ripple

Figure 7: EVREF0102 Ultra-Low Noise Power Supply Module

The output voltage noise is below 1mV for all sensitive RF data converter rails. The EVREF0102A employs five high efficiency step-down switch-mode power modules with integrated inductors. The [MPM3833C](#) is a 6V, 3A, ultra-small step down power module, and the [MPM3683-7](#) is a 16V, 8A power module. Both power modules feature integrated protection functions including OCP, OVP, UVP, and OTP. Compared to the traditional LDO solution, the EVREF0102A can achieve up to an 80% efficiency improvement. The EVREF0102A analog power module also achieves ultra-low noise level to meet the specifications of the AMD Xilinx high-speed data converter by leveraging the forced continuous conduction mode (CCM) operation and implementing post passive filters. CLC passive filters are utilized for the two most sensitive ADC and DAC rails, and capacitive filters are utilized for the rest of the power rails. See the Appendix for reference.

Figure 8–11 illustrate the comparison between the traditional LDO solution with the MPS power module solution. The experimental results were collected at a AMD Xilinx lab on the ZCU1275 development kit. As shown in the figures, the noise level of the MPS power module solution is comparable to the traditional LDO solution.

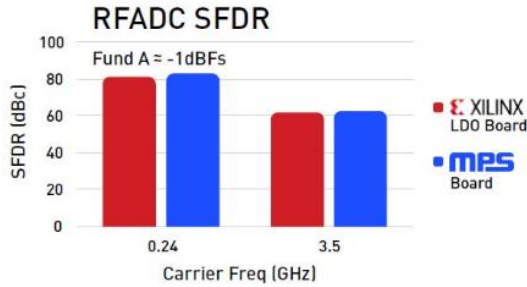


Figure 8. RFADC SFDR Result

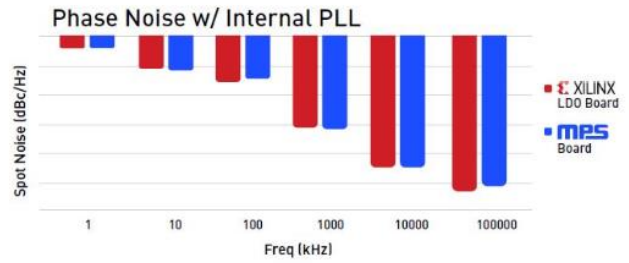


Figure 10. Comparison of Phase Noise with Internal PLL

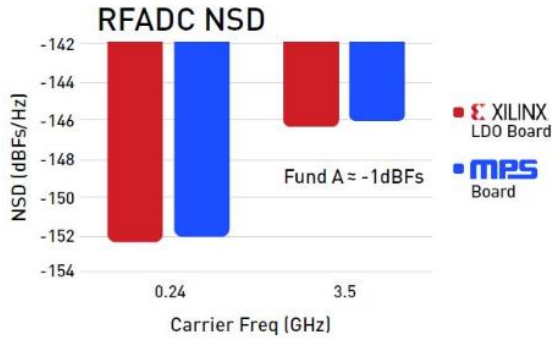


Figure 9. Comparison of RFADC NSD Results

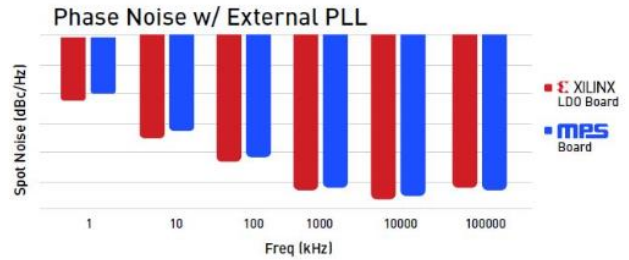


Figure 11. Comparison of Phase Noise of External PLL

Conclusion

MPS power modules provide high efficiency, full integration, and a compact power solution for AMD Xilinx FPGAs. The scalable power module offers a versatile solution for the core rail. The efficiency is improved significantly by replacing the traditional LDO with power modules for the sensitive RF data converter power rails. Two reference design boards are available from MPS with fully verified performance. The design procedure of the passive filter for minimizing the output voltage ripple for the RF data converter rails is outlined in the appendix of this application note.

Appendix: Two-Stage Filter Design

A synchronous buck converter consists of an input capacitor (C_{IN}), two switches ($S1$ and $S2$) with their body diodes, an energy storage power inductor (L), and output capacitor (C_{OUT}). The input source provides energy to the power inductor L and the load when $S1$ is turned on and $S2$ is turned off. During this period, the inductor current rises. The energy stored in the inductor is transferred to the output capacitor and load when $S2$ is on and $S1$ is off, causing the inductor current to drop. The switching behavior of the buck regulator causes the output voltage to fluctuate. The output capacitor C_{OUT} is placed at the output to smooth the output voltage under steady state. The output capacitor reduces the output voltage ripple by providing a low impedance path for the high-frequency voltage components to return to ground.

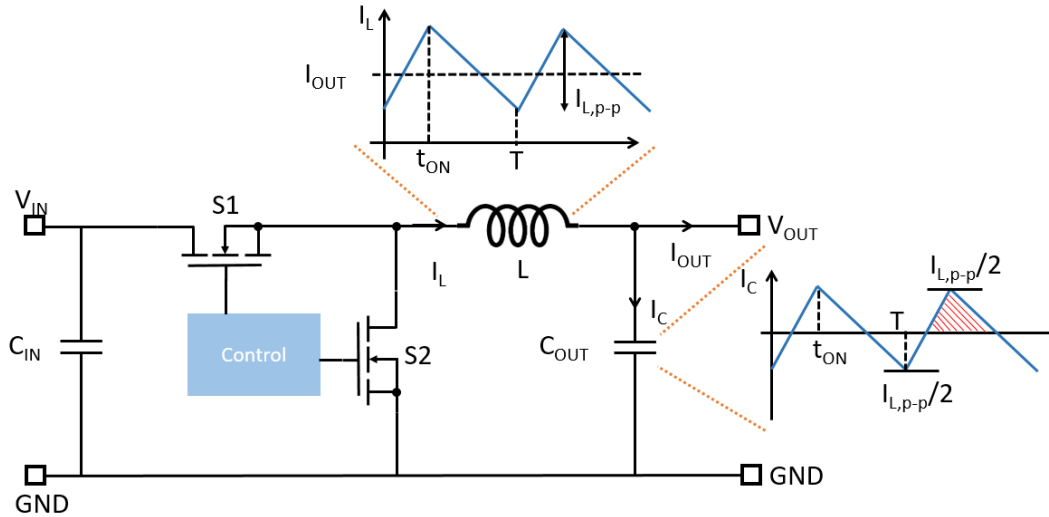


Figure 1: CCM Operation of Synchronous Buck Regulator

In the subsequent development, it is assumed the buck converter operates under continuous conduction mode (CCM) for output voltage ripple minimization. The inductance of L is designed to meet the inductor current ripple requirement. The minimum inductance of L is determined as:

$$L_{Min} = \frac{(V_{IN} - V_{OUT})D}{I_{L,p-p}f_{SW}} \quad (1)$$

Where V_{IN} and V_{OUT} represent the input and output voltage, respectively, $D = \frac{V_{OUT}}{V_{IN}}$ represents the duty ratio, $I_{L,p-p}$ is the peak-to-peak current ripple of the inductor, and f_{SW} represents the switching frequency of the converter. Typically, the peak-to-peak inductor current ripple is selected as 20-40% of the output DC current.

The output capacitance is selected to ensure that the output ripple is below the specified peak-to-peak value. For a single stage capacitive filter, a minimum output voltage ripple of 1mV to 2mV can be achieved.

Under steady state, the net electric charge delivered to the capacitor is zero within one switching period. The capacitor charge of the shaded area in Figure 1 is calculated as:

$$\Delta Q_C = \frac{T I_{L,p-p}}{4 \cdot 2} \quad (2)$$

Where T is the period of one switching cycle. By definition, the capacitor charge in a given period can also be expressed as:

$$\Delta Q_C = C \Delta V_C \quad (3)$$

For equations (2) and (3), the minimum capacitance to achieve the required output peak-to-peak voltage ripple, $V_{OUT,p-p}$, is determined as:

$$C_{Min} = \frac{I_{L,p-p}}{8f_{SW}\Delta V_{C,p-p}} \quad (4)$$

Ideally, the noise shunt capability can be increased by paralleling more output capacitors. In practical use, the output capacitors are placed laterally on a PCB. Adding more output capacitors on a PCB would introduce additional parasitic inductance and AC resistance to the shunt path and thus reduce the effectiveness of bypassing the switching noise.

A typical PCB layout of a MPS power module, which integrates optimized inductors to simplify the power converter design, is shown in Figure 2. In the PCB layout of the [MPM3833C](#), a wide copper plane is used for the output power path to minimize power losses. The output capacitors are placed along the output current path. As shown in the figure, as more capacitors are placed on the output plane, the distance from the additional capacitor to the output pin of the power module increases. Consequently, more parasitic inductance is involved in the output capacitor that is farther away from the power module. Adding more output capacitance become less and less effective, and eventually, the shunt loop is dominated by parasitic inductance.

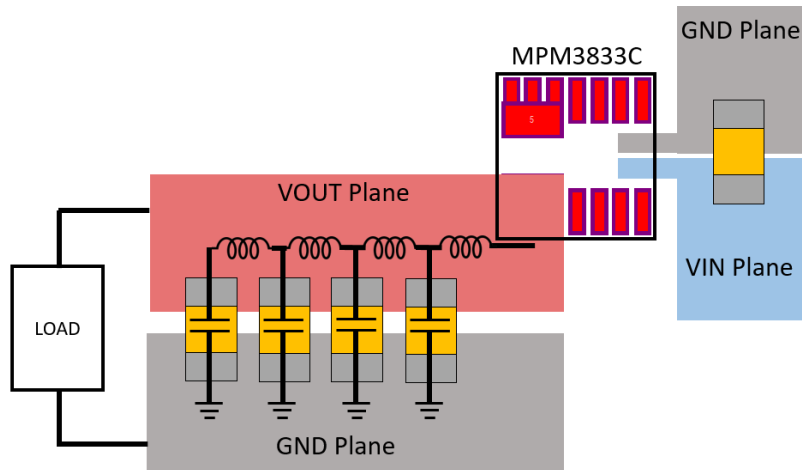


Figure 2: Typical PCB Layout for the MPM3833C Power Module

To demonstrate the impact of loop parasitic inductance, an MPM3833C with various output capacitors is simulated using Simplis. It is assumed that each additional output capacitor introduces an additional 0.5nH parasitic inductance to the bypassing loop. Figure 3 illustrates the output ripple of the power module with one 22μF capacitor. The bypassing capacitor effectively reduces the output ripple to about 3mV at 5V input, 1.2V output, and 2A load.

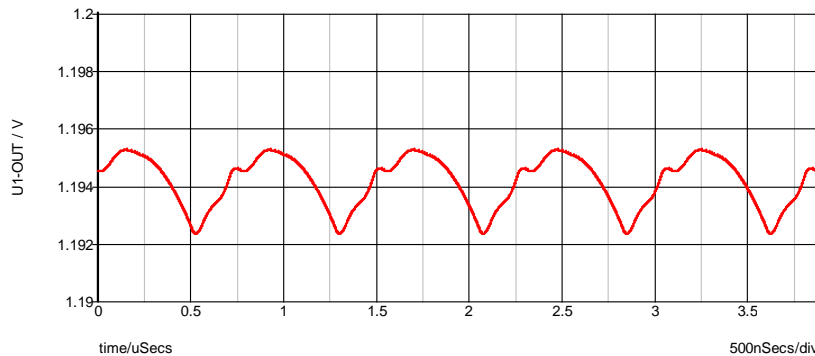


Figure 3: Output Voltage Ripple of the MPM3833C with One 22μF Output Capacitor

To further reduce the output voltage ripple, 1 additional 22 μ F output capacitor is placed at the output. Since the new capacitor has to be placed farther away from the power module, the parasitic inductance involved with the new capacitor is 1nH. The simulated output voltage ripple is shown in Figure 4 (a) where the output voltage ripple is reduced to 2mV. Compared to the waveform shown in Figure 3, where one 22 μ F output capacitor effectively brings down the output voltage ripple to 3mV, the additional 22 μ F capacitor is less effective. Fig. 4 (b) shows the output voltage ripple with one more 22 μ F capacitor (total of 4x22 μ F). The last 22 μ F capacitor involves 1.5nH parasitic inductance in its bypassing loop. As shown in the figure, the output ripple reduction achieved by the additional 22 μ F capacitor is less than 5%, compared to the case when 3x22 μ F is used.

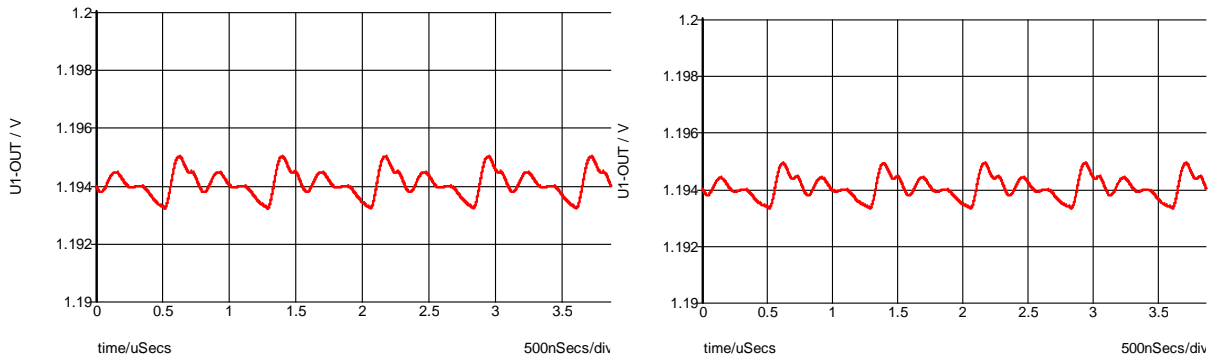


Figure 4: Output Voltage Ripple of the MPM3833C with (a) 4x22 μ F Output Capacitors and (b) 5x22 μ F Output Capacitors

As demonstrated in Figure 3 and Figure 4, the parasitic inductance introduced by the PCB copper/trace becomes dominant as more output capacitors are placed on the PCB. Eventually, the benefit of adding more capacitors is negated by the additional parasitic inductance added in the loop.

Second-Stage Filter Design

Typically, the shunt output capacitor can effectively reduce the output voltage ripple to 1mV. Beyond this point, a second stage output filter is required to achieve a smaller output voltage ripple (sub 1mV voltage ripple can be achieved). Fig. 5 illustrates a second stage LC filter, which is cascaded to the first stage output capacitors. The second stage filter consists of one filter inductor and its series resistor DCR, a bypassing capacitor branch, and a damping branch. The LC filter works by creating a high impedance to the output. The filtering inductor L_f is resistive at the intended high frequency range and dissipates the noise energy in the form of heat. The inductor combines with additional shunt capacitors to form a low-pass LC filter network.

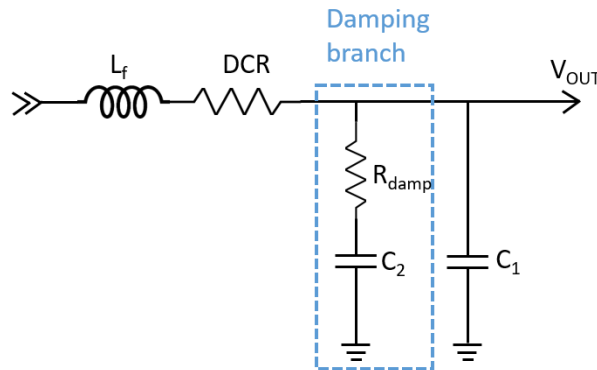


Figure 5: Second-Stage LC Filter with Parallel Damping Branch

The second stage filter is very effective on reducing the output voltage noise when properly designed. It is crucial to size the component of the second stage LC filter for the intended frequency band. The first step of the design procedure involves choosing the first stage output capacitor based on Equation (4). 5mV to 10mV output voltage ripple is typical for the first stage design. Usually a 10-22μF capacitor is sufficient. The capacitor COUT of the first stage has to be smaller than the bypassing capacitor C1 of the second stage to ensure system stability.

Once the first stage COUT is determined, and the specified output voltage ripple (at given frequency) is given, the required attenuation of the second stage LC filter can be determined as:

$$A_{0,dB} = 20 \log \frac{V_{o,p-p}}{V_{1,p-p}} \quad (5)$$

Where $V_{1,p-p}$ represents the peak-to-peak voltage ripple at the output capacitor, and $V_{o,p-p}$ represents the peak-to-peak output voltage (after the second stage filter). Using phasor analysis, the amplitude of the gain of the LC filter is determined as:

$$|H(f)| = \frac{1}{\sqrt{[1-(2\pi f)^2 L_f C_1]^2 + (\omega R_{DC} C_1)^2}} \quad (6)$$

Note that the impedance of the damping branch, which consists of a large series resistor, is much larger than the bypassing branch at the switching frequency. Thus the filter shown in Figure 5 is approximated as a second order RLC filter. The cut-off frequency of the filter is determined as:

$$f_0 = \frac{1}{2\pi \sqrt{L_f C_1}} \quad (7)$$

Typically, an inductor with 0.22μH to 1μH of inductance can be selected to achieve the required output ripple. The inductor should be selected to have minimal DCR as the serious resistance increases power dissipation and reduces the output voltage regulation. It should be noted that as the DC current increases, the core material of the inductor becomes saturated, which reduces the inductance of the inductor. Care should be taken to ensure that the inductance is high enough at the rated DC current.

Once the filtering inductor is selected, its DCR can be extracted from the datasheet. The second stage LC filter, which is a second order filter, provides 40db per decade roll-off after the cutoff frequency. The attenuation at given frequency can be estimated as:

$$A(f) = -40 \log \left(\frac{f}{f_0} \right) \text{ dB} \quad (8)$$

Using the attenuation calculated in equation (5), the required cut-off frequency is determined as:

$$f_0 = \frac{f}{10^{\frac{A_0}{-40}}} \quad (9)$$

Subsequently, the required bypassing capacitance C1 is determined as:

$$C_1 = \frac{1}{4\pi^2 f_0^2 L_f} \quad (10)$$

Ceramic capacitors should be used as the bypassing capacitor for low ESR and ESL. It should be noted that the capacitance of ceramic capacitors experience significant de-rating at DC bias voltage. Figure 6 illustrates the DC de-rating curve of a Murata 0805 ceramic capacitor, which is rated at 6.3V. As shown in the figure, at the full rated DC bias voltage, the capacitance drops to 20% of the nominal value. The bypassing capacitor should be selected at the nominal DC bias voltage to factor in the de-rating.

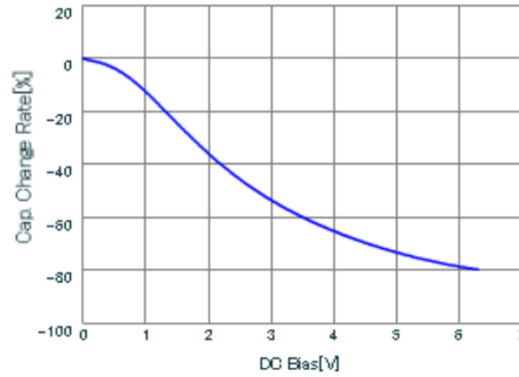


Figure 6: Typical Ceramic Capacitor Derating Curve at DC Bias

Damping

The second stage LC filter may introduce resonance peaking if not properly damped. The resonance between the filtering inductor and bypassing capacitor may amplify the output ripple and create undesired ringing at load transient. Figure 7 (a) shows the output voltage of an underdamped converter system with the second stage LC filter. Initially, the system operates under steady state. At $t = 200\mu\text{s}$, a load transient from 1A to 2A is initiated, which causes the output voltage to ring. Figure 7 (b) illustrates the output voltage and current under load transient of an overdamped second stage filter. To avoid undesired ringing at load transient, the second stage LC filter resonance must be properly damped. In most designs, the second stage filter will be placed outside of the control loop to avoid control stability issues. Consequently, the damping has to be achieved by passive components (additional damping resistors).

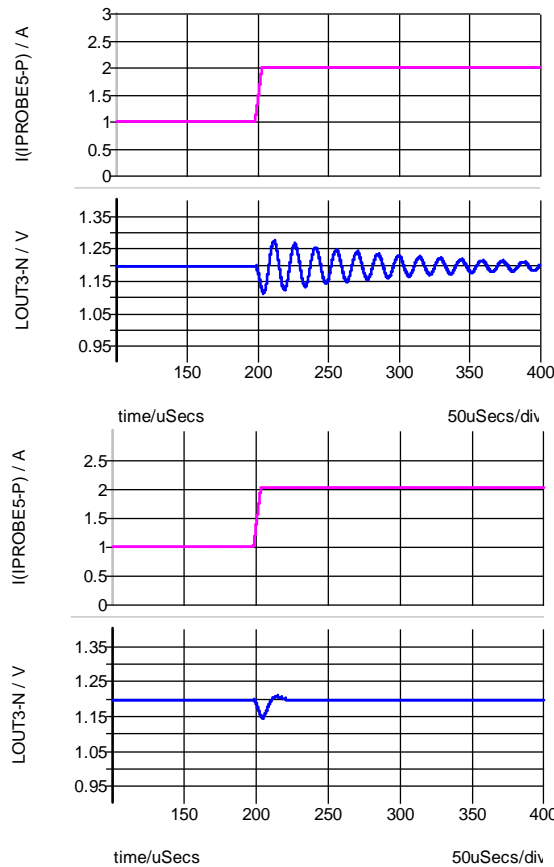


Figure 7: Step Response of (a) Underdamped LC Filter and (b) Overdamped LC Filter

The filtering inductor usually includes a parasitic DC resistance in series with the inductor. This DCR provides damping to the network. However, to provide enough damping for a series RLC circuit, the series resistance has to satisfy $R_{DC} > 2\sqrt{\frac{L_f}{C_1}}$. In most cases, the DCR alone cannot provide sufficient damping. To this end, a RC damping network is inserted in parallel with the bypassing capacitors to damp the resonant circuit along with the series DCR resistor.